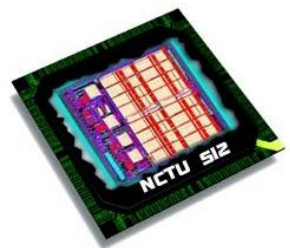


Advanced Sequential Circuit Design

NYCU-EE IC Lab Fall 2023

Lecturer : Jia-Yu, Lee



Outline

- ✓ **Section 1- Timing**
- ✓ **Section 2- Designware**



Outline

✓ **Section 1- Timing**


- Setup/hold time
- Pipeline

✓ **Section 2- Designware**



Recall

Des/Clust/Port	Wire Load Model	Library	
CNC	umc18_wl10	slow	
Point	Incr	Path	
clock clk (rise edge)	0.00	0.00	
clock network delay (ideal)	1.00	1.00	
cnt_reg_0_/CK (DFFHQX4)	0.00	1.00	
cnt_reg_0_/Q (DFFHQX4)	0.47	1.47 r	
U784/Y (INVX8)	0.11	1.58 f	
U767/Y (NAND2X4)	0.15	1.73 r	
U786/Y (NOR2X4)	0.08	1.80 f	
U376/Y (BUF8)	0.20	2.01 f	
U374/Y (NAND2XL)	0.21	2.21 r	
U772/Y (OAI211X1)	0.23	2.44 f	
U771/Y (NAND2BX4)	0.28	2.72 f	
U832/Y (XNOR2X4)	0.30	3.01 r	
U366/Y (BUF8)	0.21	3.22 r	
U834/Y (NAND2X4)	0.14	3.36 f	
U732/Y (BUF20)	0.19	3.56 f	
U738/Y (OAI2BB2X4)	0.16	3.72 r	
U850/CO (ADDFHX4)	0.49	4.21 r	
U852/S (ADDFHX4)	0.38	4.59 r	
U860/S (ADDFHX4)	0.43	5.02 r	
U341/Y (NOR2X2)	0.15	5.17 f	
U862/Y (NOR2X4)	0.22	5.39 r	
U744/Y (NAND2X4)	0.13	5.52 f	
U742/Y (OAI21X4)	0.32	5.84 r	
U331/Y (BUF8)	0.20	6.04 r	
U739/Y (AOI21X4)	0.12	6.16 f	
U972/Y (NAND2X1)	0.19	6.35 r	
U317/Y (OAI2BB1X1)	0.14	6.49 f	
F_reg_16_/D (DFFHQX1)	0.00	6.49 f	
data arrival time		6.49	
clock clk (rise edge)	6.00	6.00	
clock network delay (ideal)	1.00	7.00	
clock uncertainty	-0.10	6.90	
F_reg_16_/CK (DFFHQX1)	0.00	6.90 r	
library setup time	-0.41	6.49	
data required time		6.49	
data required time		6.49	
data arrival time		-6.49	
slack (MET)		0.00	

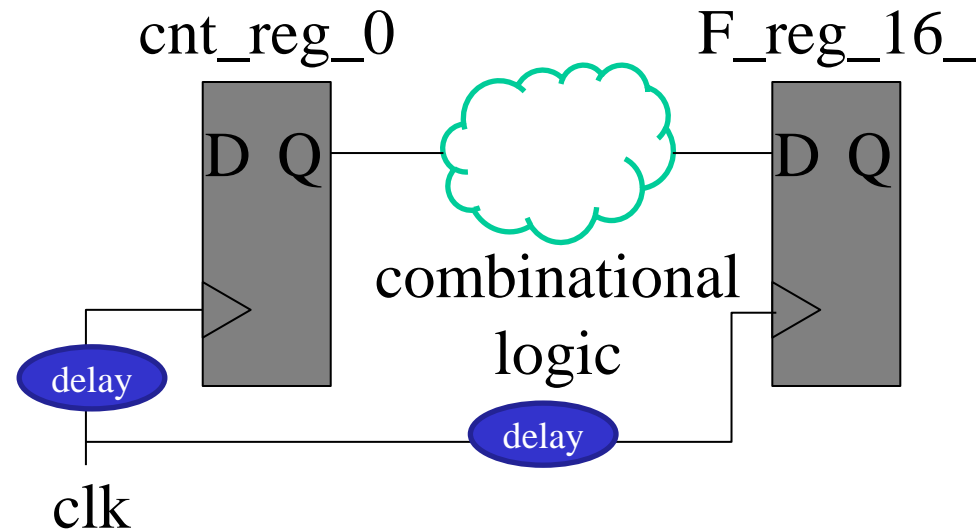

Recall


✓ Launch Edge:

- The clock rising edge used by Register 1 for generating data

✓ Latch Edge:

- The clock rising edge used by Register 2 for receiving data will introduce a delay of one clock cycle from Launch Edge

Launch Edge & Latch Edge

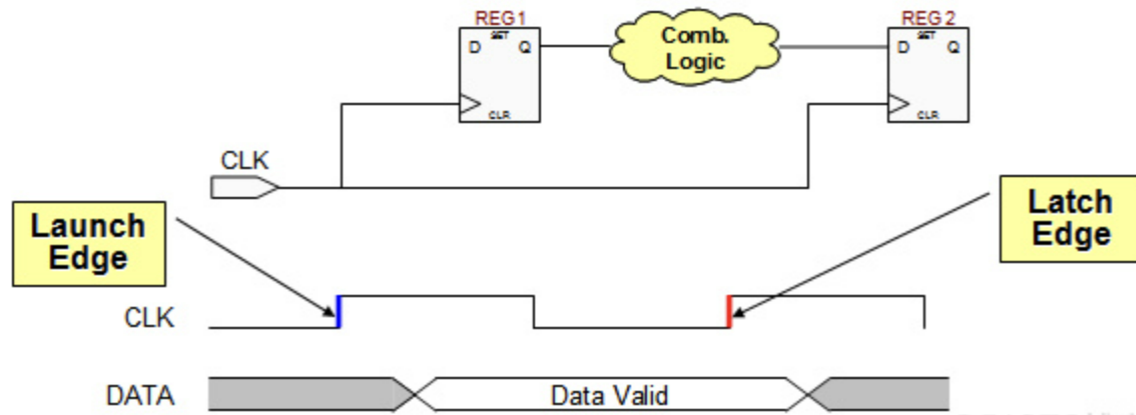

@51CTO博客



Timing Issue



✓ Terminology

- Setup time (t_{setup})

The time that the input signal must be stabilized **before** the clock edge.


- Hold time (t_{hold})

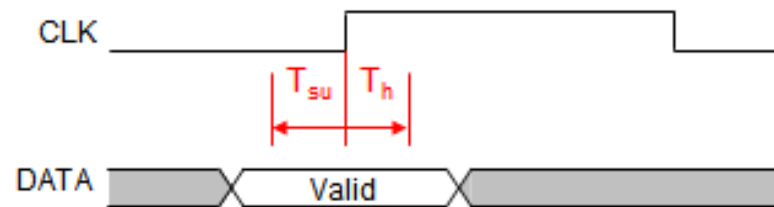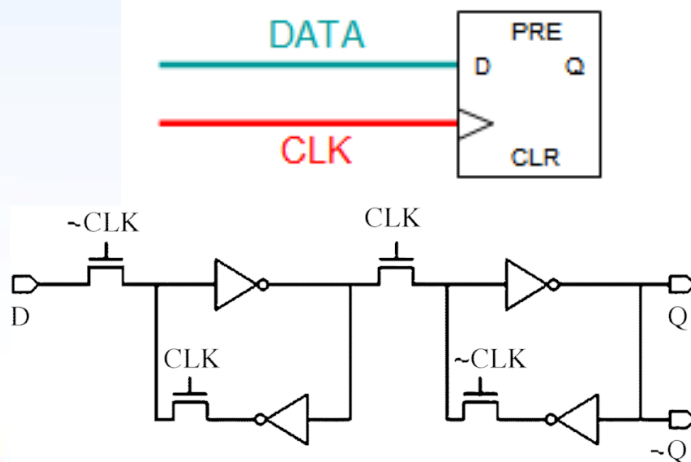The time that the input signal must be stabilized **after** the clock edge.



Timing Issue


✓ Metastability

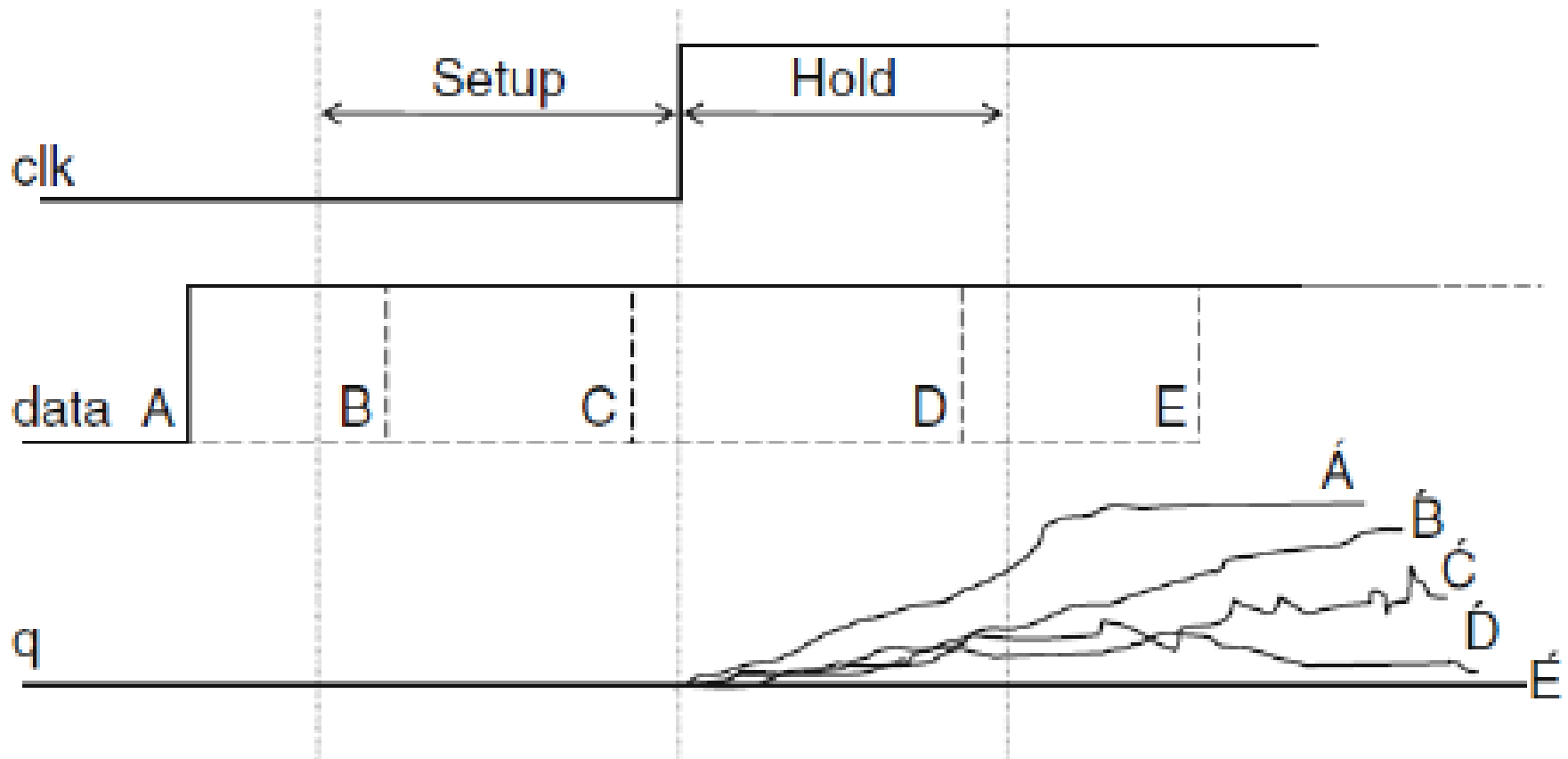

Timing Check (1/2)


✓ Setup time check

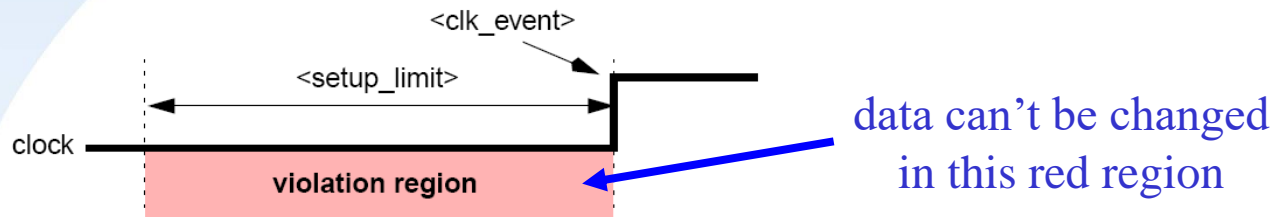- The tool determines whether a data signal **remains stable** for a minimum specified time (i.e., violation region) **before** a transition in an enabling signal, such as a clock event.



✓ Hold time check

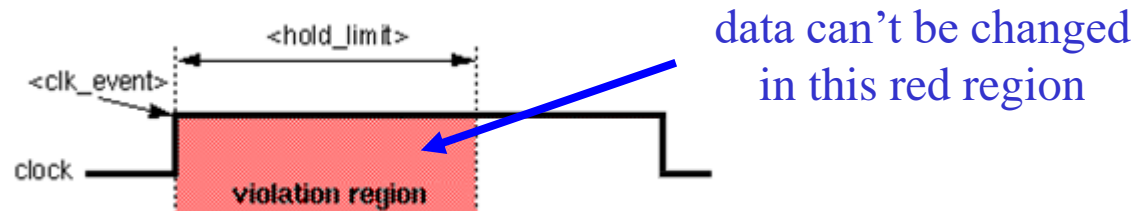- The tool determines whether a data signal **remains stable** for a minimum specified time (i.e., violation region) **after** a transition in an enabling signal, such as a clock event.



Timing Check (2/2)

✓ Timing report: setup time

clock CLK_1 (rise edge)	2.00	2.00
clock network delay (ideal)	2.00	4.00
clock uncertainty	-0.50	3.50
IN_A_reg[0]/CK (EDFFXL)	0.00	3.50 r
library setup time	-0.42	3.08
data required time		3.08

data required time		3.08
data arrival time		-3.08

slack (MET)		0.00

✓ Timing report: hold time

Slacks should be **MET!**
(non-negative)

clock CLK_2 (rise edge)	0.00	0.00
clock network delay (ideal)	4.00	4.00
clock uncertainty	1.00	5.00
IN_B_reg[20]/CK (EDFFXL)	0.00	5.00 r
library hold time	-0.19	4.81
data required time		4.81

data required time		4.81
data arrival time		-4.82

slack (MET)		0.01




Terminology

✓ Data Arrival Time

- The time at which data actually arrives at the input D of Register 2

Data Arrival Time

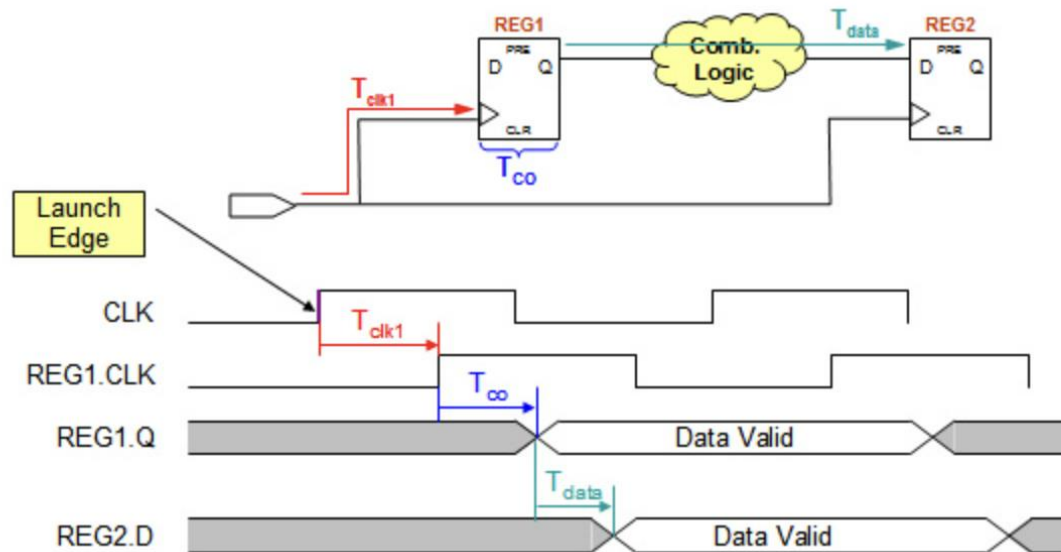

$$\text{Data Arrival Time} = \text{launch edge} + T_{clk1} + T_{co} + T_{data}$$


@51cto博客

Terminology

✓ Clock Arrival Time

- The actual time at which the clock signal arrives at the input of Register 2

Clock Arrival Time

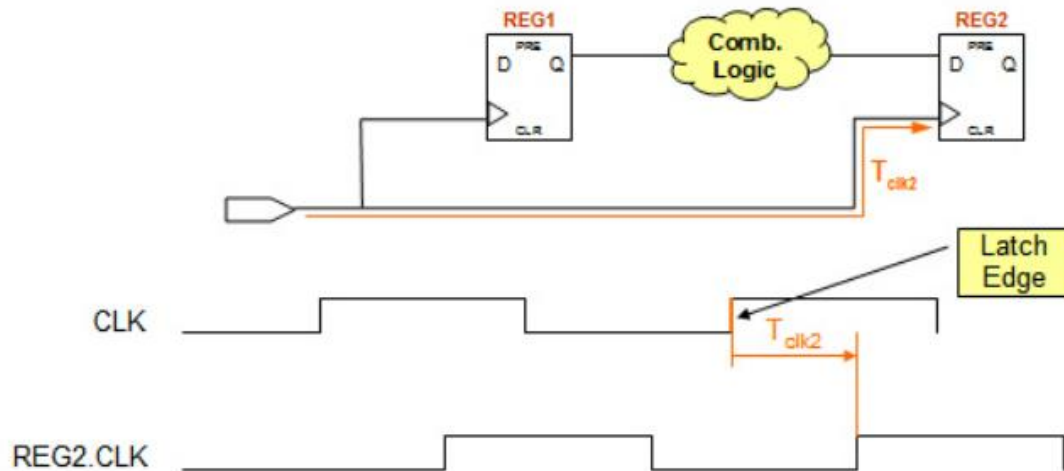


$$\text{Clock Arrival Time} = \text{latch edge} + T_{clk2}$$

@51CTO博客

Terminology

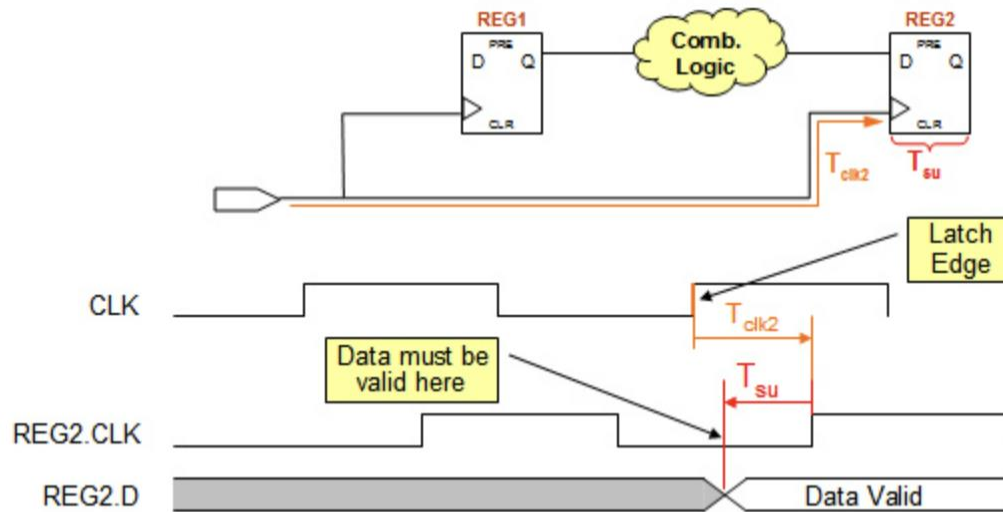- ✓ **Data required Time (setup time)**
 - The latest time by which the data must be ready




$$\text{Data Required Time} = \text{Clock Arrival Time} - T_{su} - \text{Setup Uncertainty}$$

Terminology

✓ Data required Time (hold time)

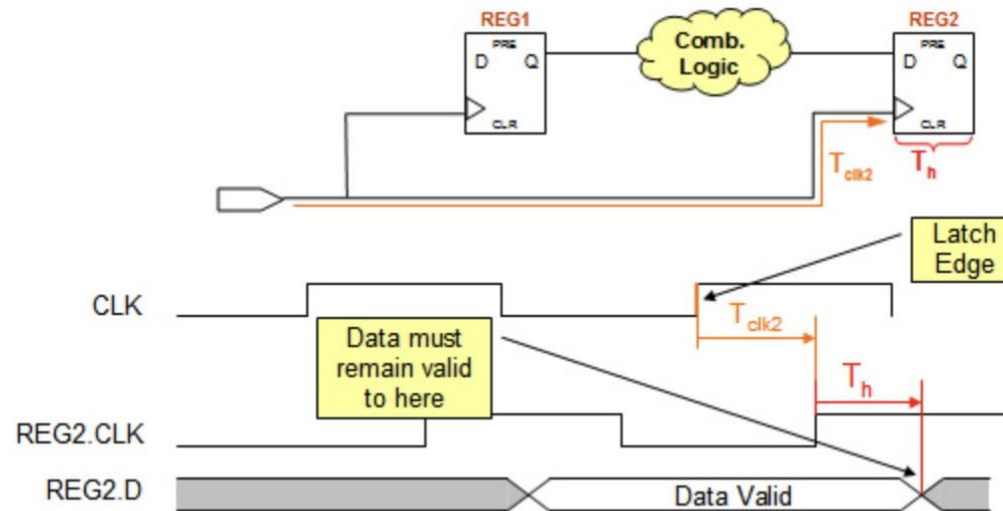
- Until what time at least does the data need to be maintained



$$\text{Data Required Time} = \text{Clock Arrival Time} + T_h + \text{Hold Uncertainty}$$

@51C10博客

Setup Slack

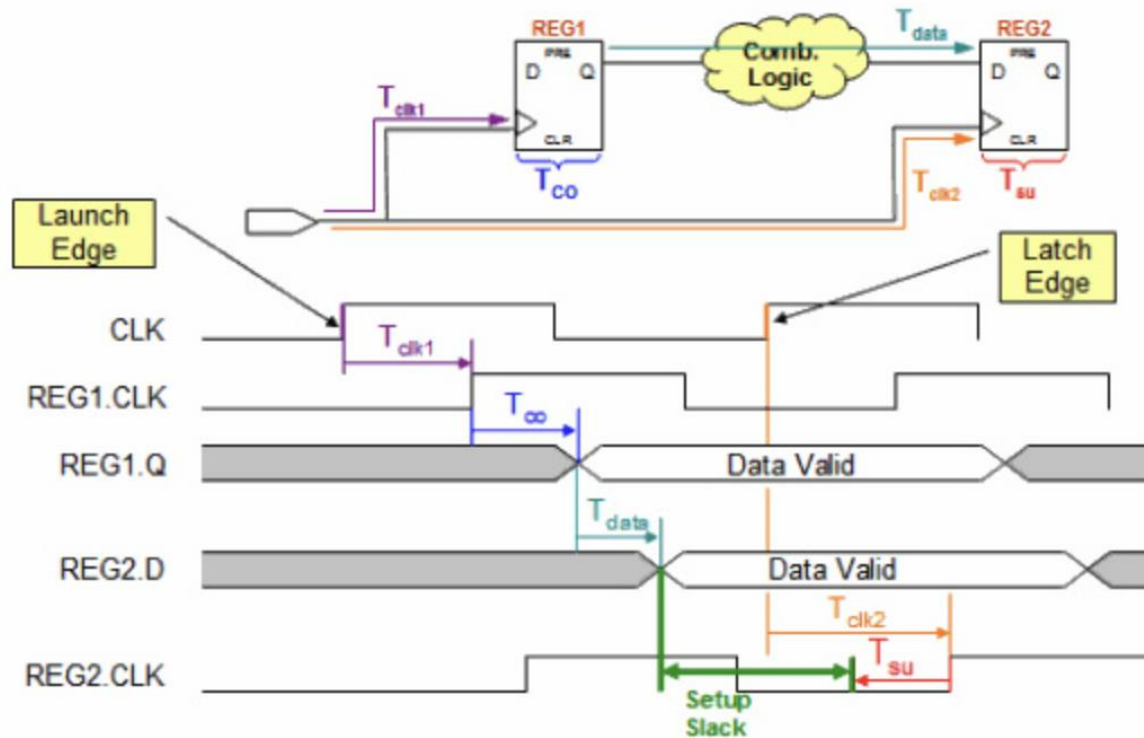

$$\text{Setup Slack} = \text{Data Required Time} - \text{Data Arrival Time}$$

Positive slack


Timing requirement met

Negative slack

Timing requirement not met

©ICTO 博客

Hold Slack

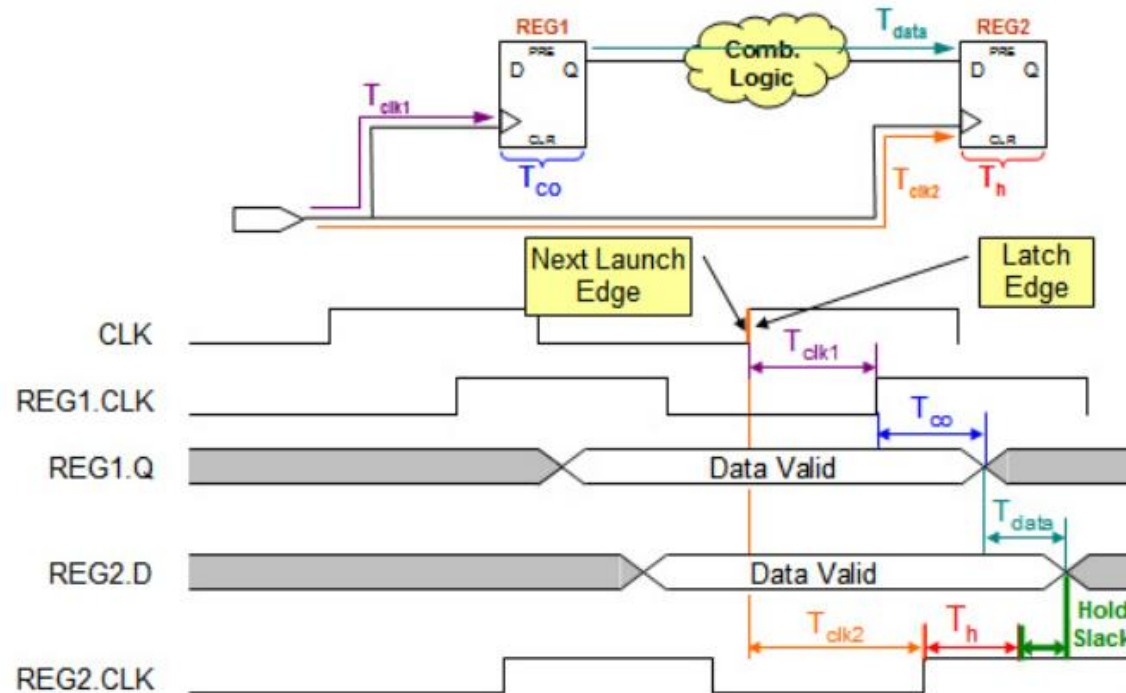

Hold Slack = Data Arrival Time – Data Required Time

Positive slack

Timing requirement met

Negative slack

Timing requirement not met

@51CTO博客



Timing Issue

✓ Terminology

– Contamination delay


The minimum amount of time from an **input changes** until **any output starts to change** its value.

- Clk-to-Q contamination delay (t_{ccq})
- Logic contamination delay (t_{cd})



– Propagation delay

The maximum amount of time from **input changes** until **all output reaches steady state**.

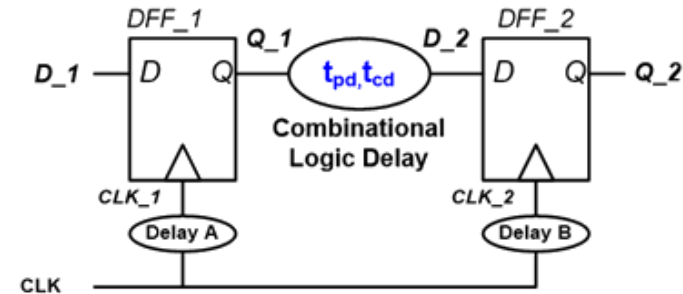- Clk-to-Q propagation delay (t_{pcq})
- Logic propagation delay (t_{pd})




Timing Issue

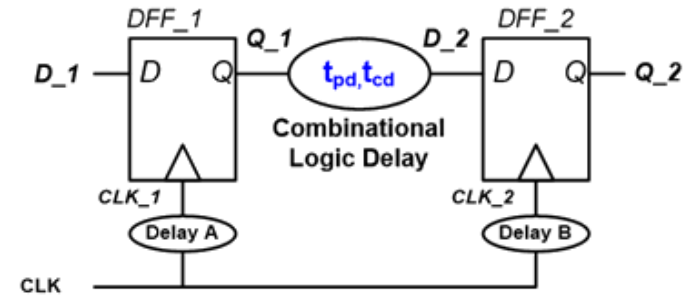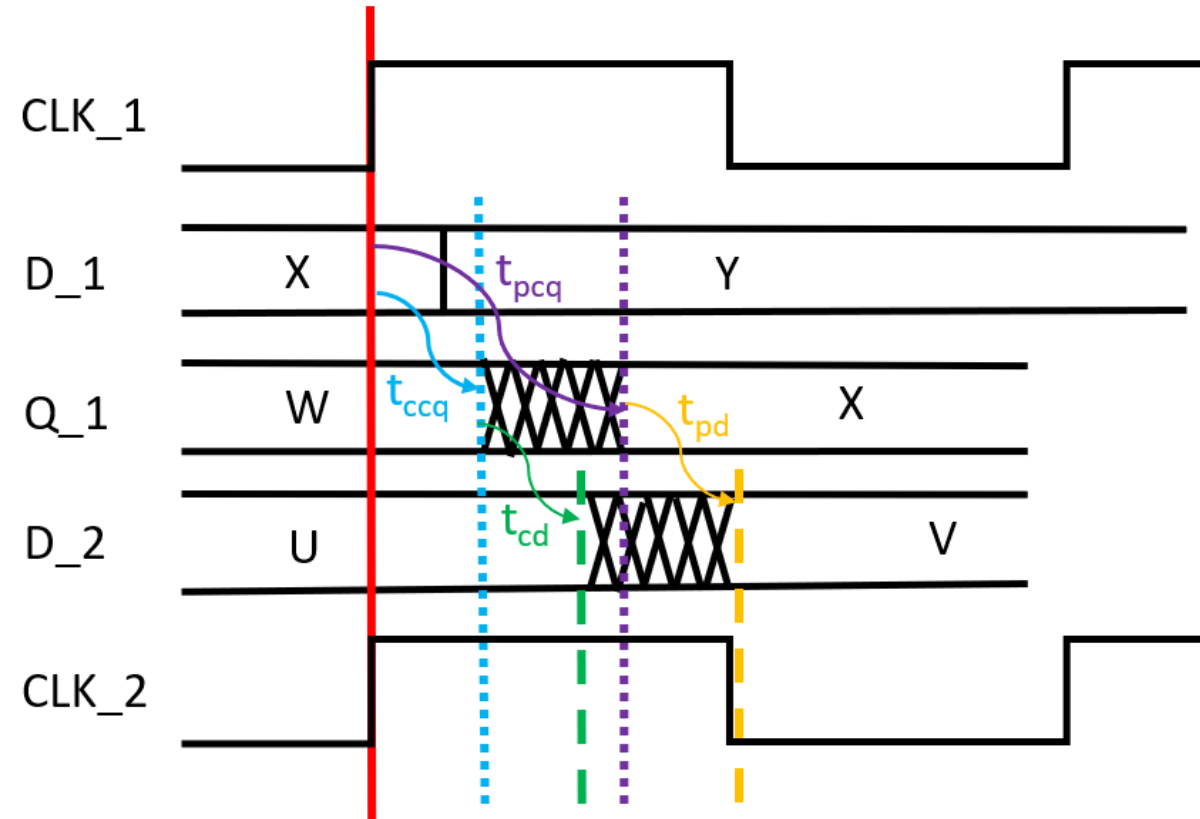

Setup Time Criterion

✓ **Setup time criterion:** $(T_{cycle} + t_{skew}) > (t_{pcq} + t_{pd} + t_{setup})$

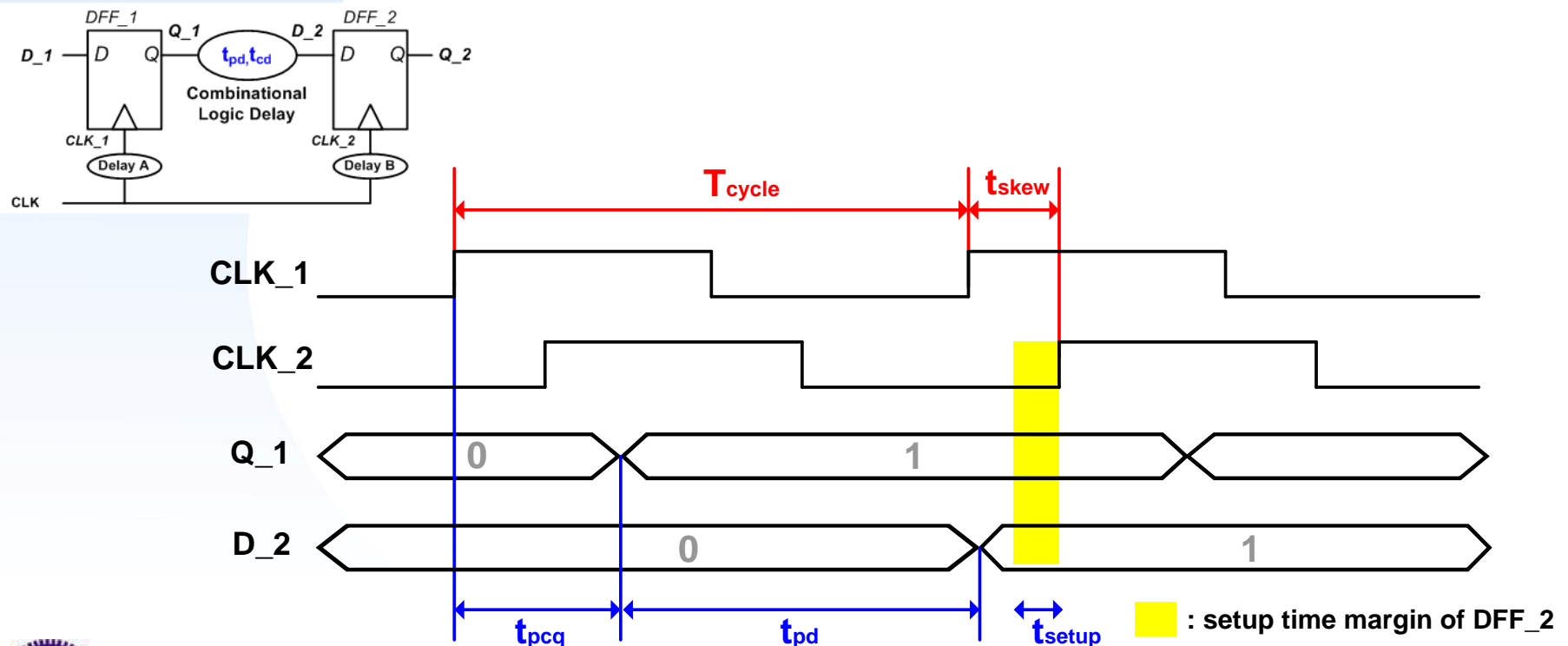
- data required time = $T_{cycle} + t_{skew} - t_{setup}$
- data arrival time = $t_{pcq} + t_{pd}$
- Slack = data required time - data arrival time



Setup Time Criterion

✓ **Setup time criterion:** $(T_{cycle} + t_{skew}) > (t_{pcq} + t_{pd} + t_{setup})$


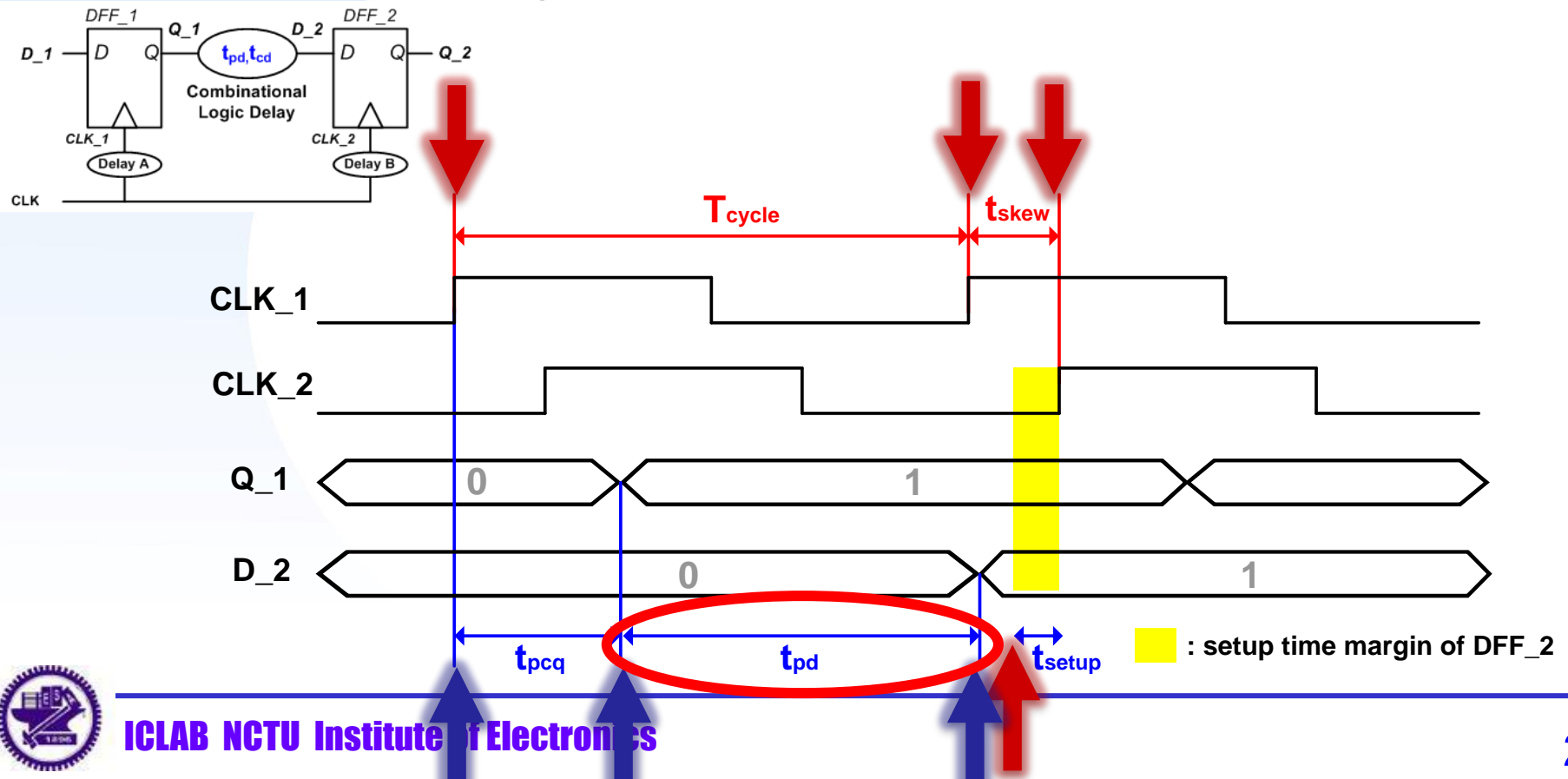
- data required time = $T_{cycle} + t_{skew} - t_{setup}$
- data arrival time = $t_{pcq} + t_{pd}$
- Slack = data required time - data arrival time



Hold Time Criterion

✓ **Hold time criterion:** $(t_{ccq} + t_{cd}) > (t_{hold} + t_{skew})$

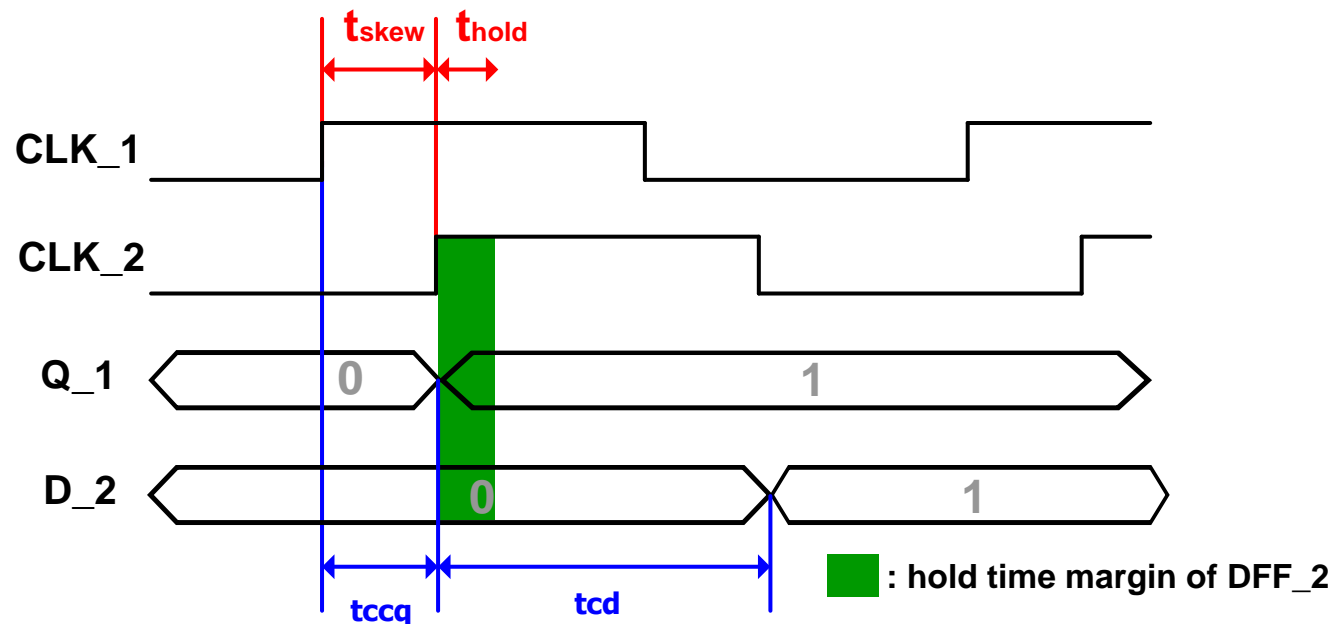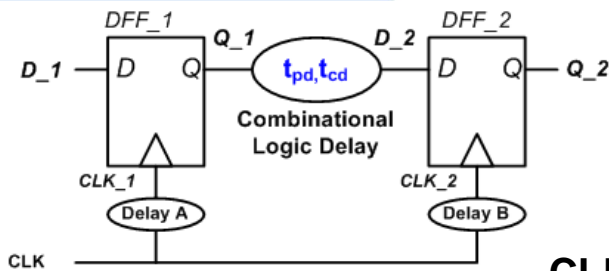
- data required time = $t_{skew} + t_{hold}$
- data arrival time = $t_{ccq} + t_{cd}$
- Slack = data arrival time – data required time



Hold Time Criterion

✓ **Hold time criterion:** $(t_{ccq} + t_{cd}) > (t_{hold} + t_{skew})$

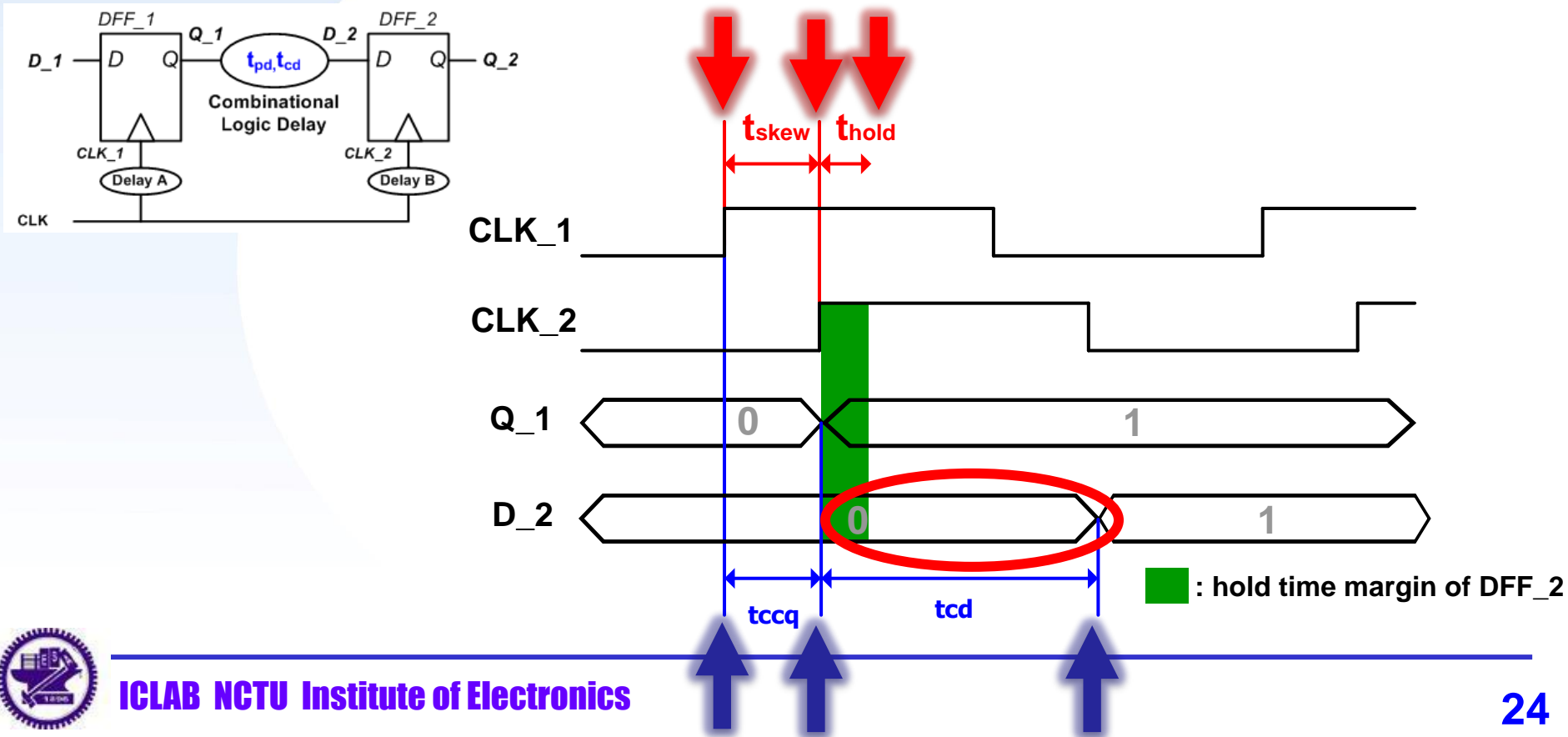- data required time = $t_{skew} + t_{hold}$
- data arrival time = $t_{ccq} + t_{cd}$
- Slack = data arrival time – data required time



When Timing Violation Occurs...

- ✓ **Adjust data path to meet the constraints**
 - Setup violation → too many works in one cycle
 - Apply pipelining
 - Hold violation → insufficient delay
 - add delays to the violated path, such as buffers/inverters/Muxes
- ✓ **Increase clock period for setup violation**
- ✓ **In most practical cases, hold violations are fixed during the backend work (after clock tree synthesis)**



Outline

✓ **Section 1- Timing**

- Setup/hold time
- Pipeline

✓ **Section 2- Designware**






Trade-off between Area and Timing




Area: 1 unit

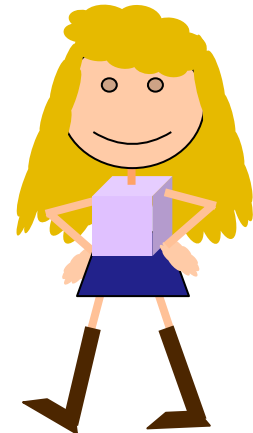 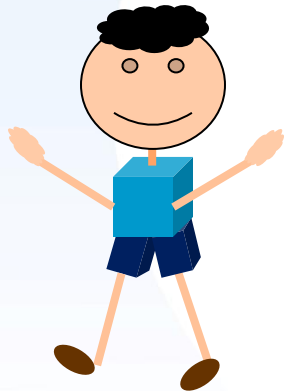
Time: 40 mins (Wash: 20 mins + Dry: 20 mins)




Trade-off between Area and Timing

 

Wash and Dry = 40 mins

 


Trade-off between Area and Timing

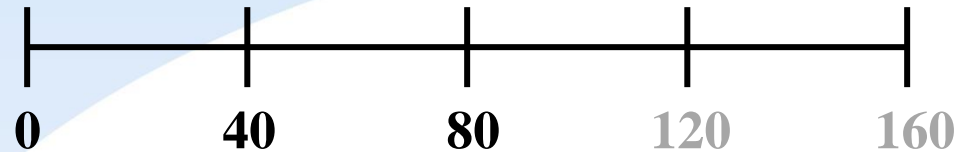

Wash and Dry = 40 mins




Trade-off between Area and Timing

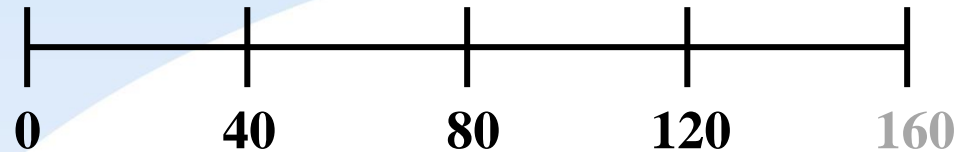


Wash and Dry = 40 mins



Trade-off between Area and Timing

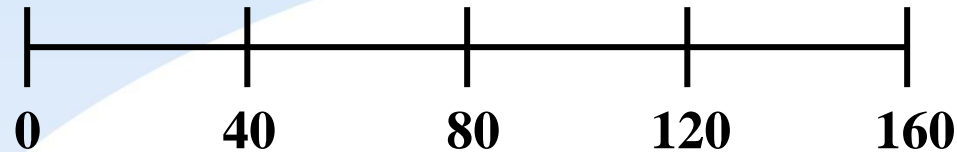


Wash and Dry = 40 mins

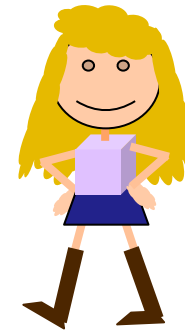

Area: 1 unit

Time: 160 mins

Trade-off between Area and Timing

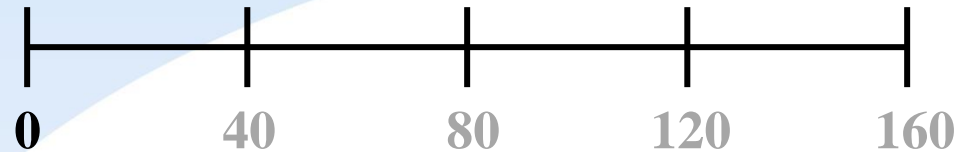

Wash and Dry = 40 mins


Area: 1 unit

Time: 160 mins




Wash and Dry = 40 mins

Trade-off between Area and Timing

 

Wash and Dry = 40 mins

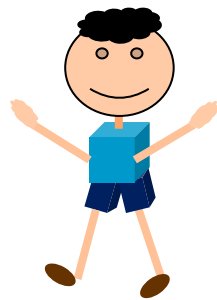

Area: 1 unit


Time: 160 mins



Wash and Dry = 40 mins




Trade-off between Area and Timing

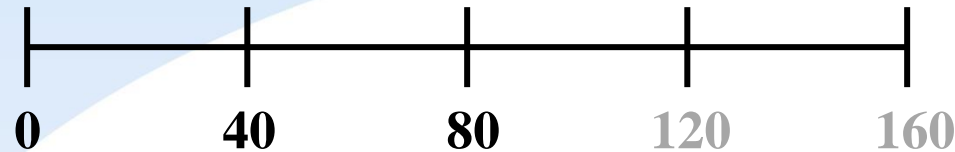

Wash and Dry = 40 mins



Wash and Dry = 40 mins


 


~~Area: 1 unit
Time: 160 mins~~



**Area: 2 units
Time: 80 mins**

Trade-off between Area and Timing

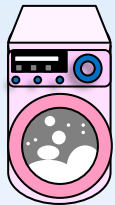 

Wash 20 mins
Area 0.7 units





Dry 20 mins
Area 0.7 units


Area: 1 unit

Time: 160 mins

Trade-off between Area and Timing

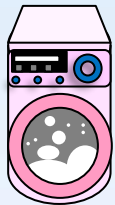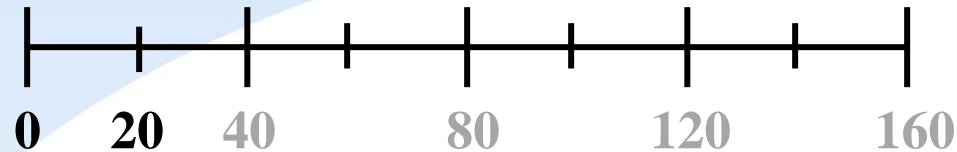

Wash 20 mins

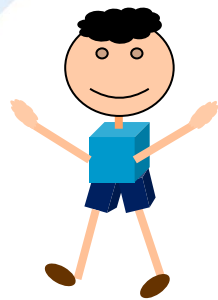



Area: 1 unit

Time: 160 mins



Dry 20 mins

Trade-off between Area and Timing

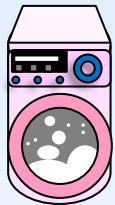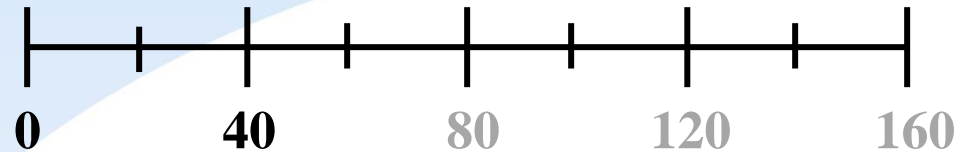

Wash 20 mins




Area: 1 unit



Time: 160 mins



Dry 20 mins

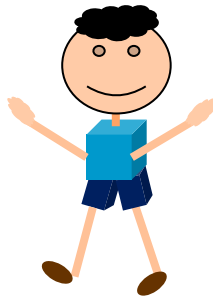

Trade-off between Area and Timing

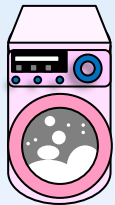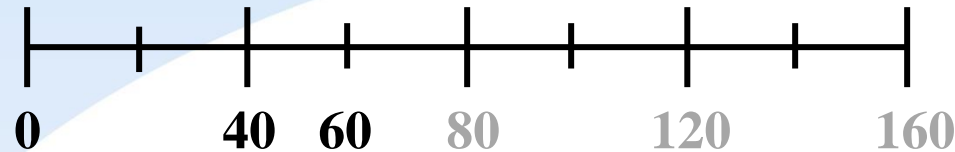

Wash 20 mins



Area: 1 unit



Time: 160 mins



Dry 20 mins




Trade-off between Area and Timing

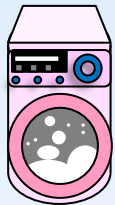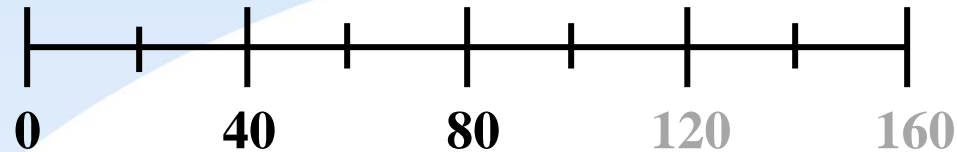

Wash 20 mins




Dry 20 mins

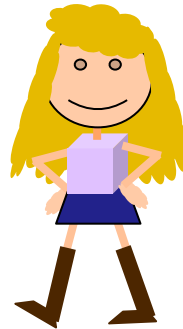

Area: 1 unit

Time: 160 mins


Trade-off between Area and Timing

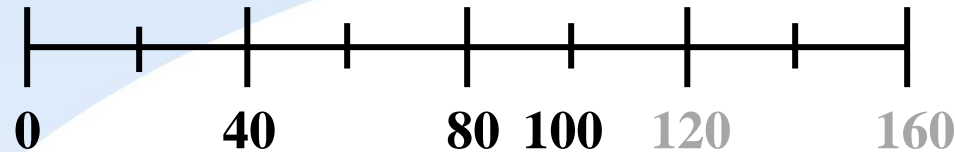

Wash 20 mins



Dry 20 mins

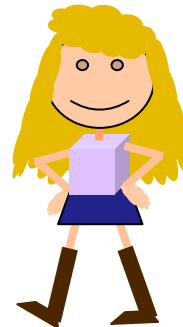


~~Area: 1 unit
Time: 160 mins~~



Area: $0.7+0.7=1.4$ units

Time: 100 mins

Trade-off between Area and Timing

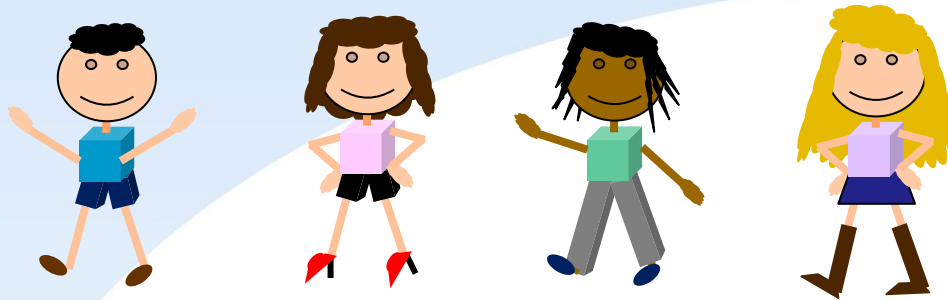


Basic




Area: 1 unit
Time: 160 mins

Parallel

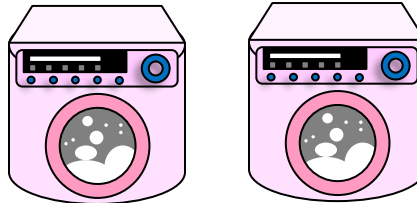

Area: 2 units
Time: 80 mins

Pipeline

 

Area: $0.7+0.7 = 1.4$ units
Time: 100 mins

Trade-off between Area and Timing

- ✓ $a [7:0]$, $b [7:0]$, $c [3:0]$, $d [3:0]$
- ✓ Q: $(a + b + c + d)$ x 1000 iterations ?

Basic

Parallel


Pipeline



Trade-off between Area and Timing

- ✓ $a [7:0]$, $b [7:0]$, $c [3:0]$, $d [3:0]$
- ✓ Q: $(a + b + c + d) \times 1000$ iterations ?

Basic

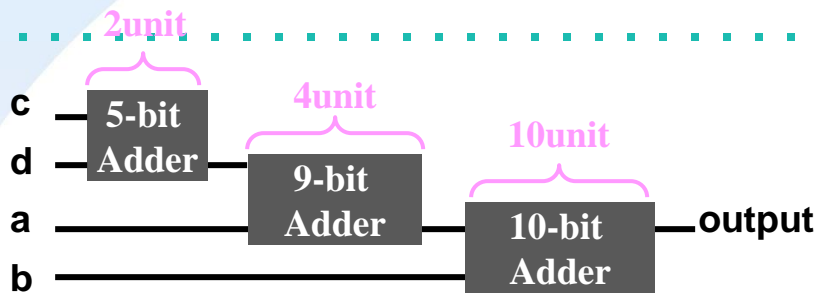

Area: 24 units
Time: $16 \times 1000 = 16000$
units

Parallel


Pipeline



Trade-off between Area and Timing


- ✓ a [7:0] , b [7:0] , c [3:0] , d [3:0]
- ✓ Q: $(a + b + c + d) \times 1000$ iterations ?

Basic

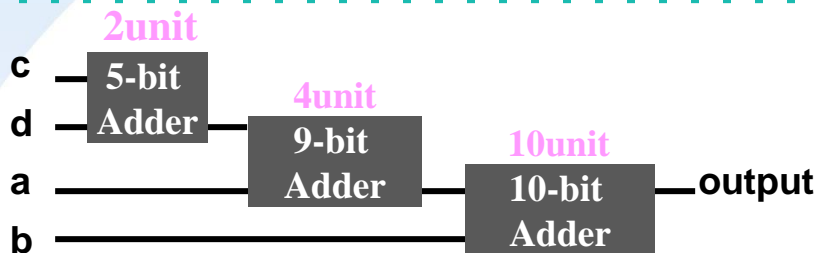

Area: 24 units
Time: $16 \times 1000 = 16000$ units

Parallel

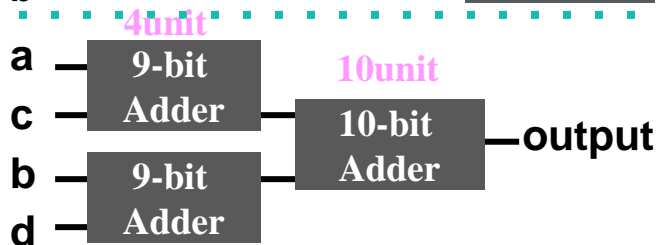

Area: 28 units
Time: $14 \times 1000 = 14000$ units


Pipeline



Trade-off between Area and Timing

- ✓ a [7:0] , b [7:0] , c [3:0] , d [3:0]
- ✓ Q: $(a + b + c + d) \times 1000$ iterations ?


Basic

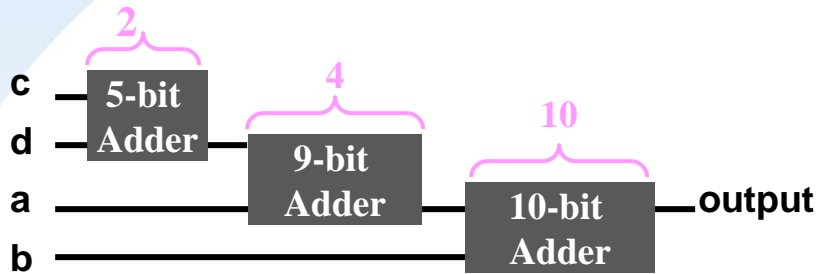

Area: 24 units

Time: $16 \times 1000 = 16000$ units


Parallel

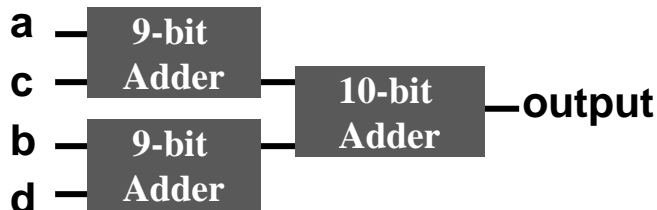


Area: 28 units

Time: $14 \times 1000 = 14000$ units

Pipeline

 


Trade-off between Area and Timing

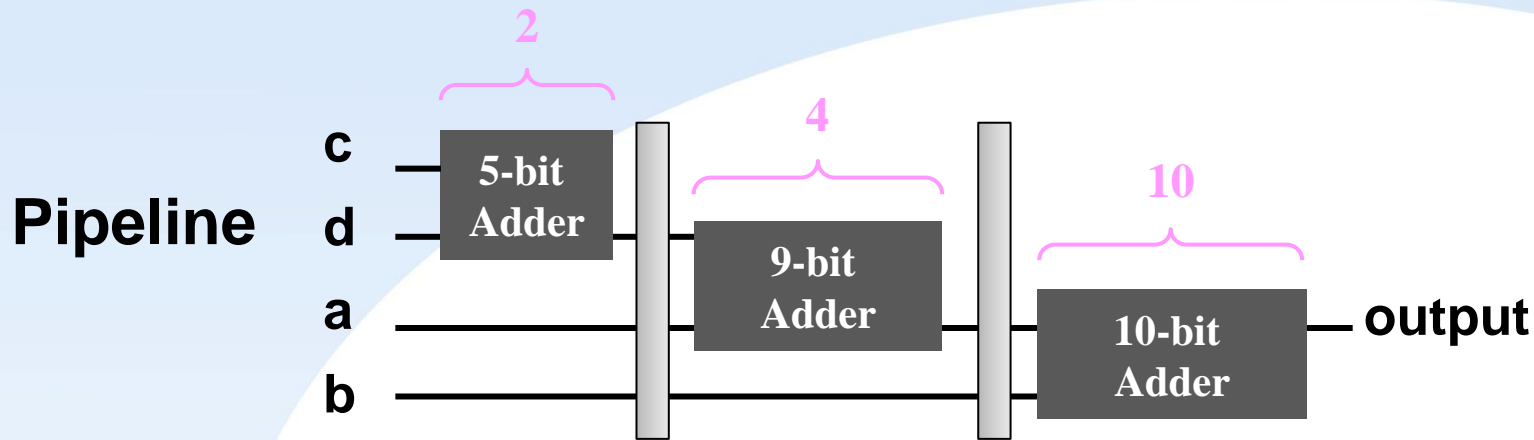

T=0	$c_1 + d_1$		

Trade-off between Area and Timing


Pipeline

 

T=0	$c1 + d1$		
T=1	$c2 + d2$	$a1 + (c1 + d1)$	


Trade-off between Area and Timing

Pipeline

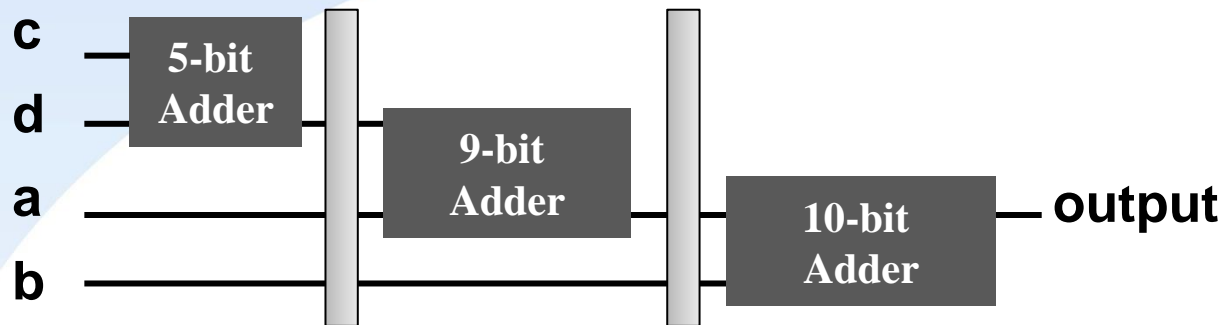

T=0	$c1 + d1$		
T=1	$c2 + d2$	$a1 + (c1 + d1)$	
T=2	$c3 + d3$	$a2 + (c2 + d2)$	$b1 + (a1 + c1 + d1)$


Trade-off between Area and Timing

 

T=0	$c1 + d1$		
T=1	$c2 + d2$	$a1 + (c1 + d1)$	
T=2	$c3 + d3$	$a2 + (c2 + d2)$	$b1 + (a1 + c1 + d1)$
T=3	$c4 + d4$	$a3 + (c3 + d3)$	$b2 + (a2 + c2 + d2)$

Trade-off between Area and Timing


Pipeline

 

T=0	$c1 + d1$		
T=1	$c2 + d2$	$a1 + (c1 + d1)$	
T=2	$c3 + d3$	$a2 + (c2 + d2)$	$b1 + (a1 + c1 + d1)$
T=3	$c4 + d4$	$a3 + (c3 + d3)$	$b2 + (a2 + c2 + d2)$
T=4		$a4 + (c4 + d4)$	$b3 + (a3 + c3 + d3)$

Trade-off between Area and Timing

Pipeline

 


T=0	$c1 + d1$		
T=1	$c2 + d2$	$a1 + (c1 + d1)$	
T=2	$c3 + d3$	$a2 + (c2 + d2)$	$b1 + (a1 + c1 + d1)$
T=3	$c4 + d4$	$a3 + (c3 + d3)$	$b2 + (a2 + c2 + d2)$
T=4		$a4 + (c4 + d4)$	$b3 + (a3 + c3 + d3)$
T=5			$b4 + (a4 + c4 + d4)$

Trade-off between Area and Timing

✓ a [7:0] , b [7:0] , c [3:0] , d [3:0]

✓ Q: $(a + b + c + d) \times 1000$ iterations ?


Basic

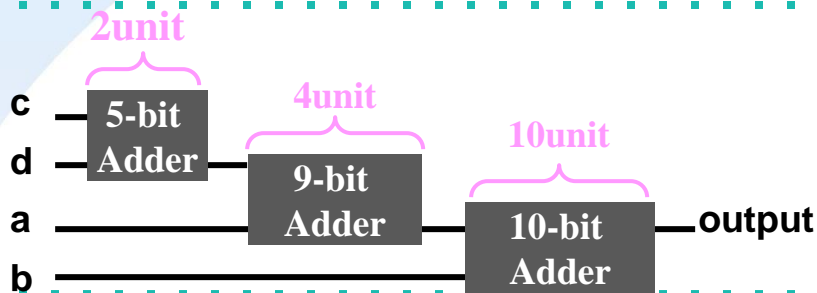

Area: 24 units

Time: $16 \times 1000 = 16000$ units


Parallel

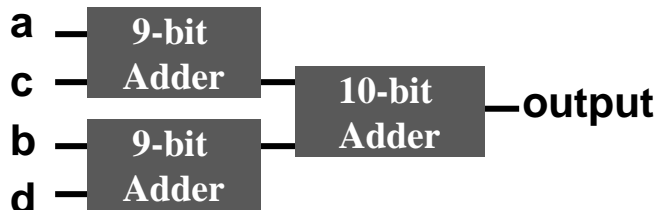

Area: 28 units

Time: $14 \times 1000 = 14000$ units

Pipeline

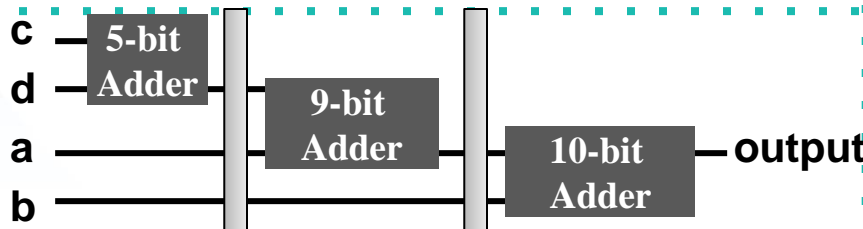

Area: 24 units+reg

Time: $10 \times 1002 = 10020$ units




Pipeline Speedup

✓ Latency of single task 😞 ✗

✓ Throughput → Speed Up 😊 ✓

- Potential speedup = Number pipe stages, if all stages are balanced.
- Pipeline rate limited by slowest stage
- Note the overhead of pipeline


Basic

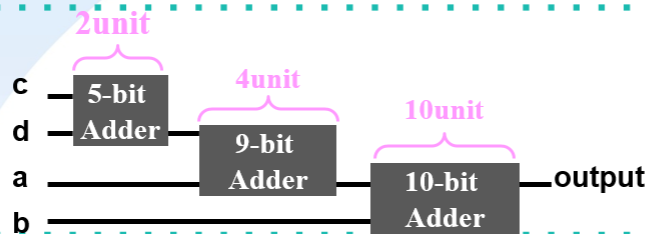

Area: 24 units

Time: $16 \times 1000 = 16000$
units

Pipeline

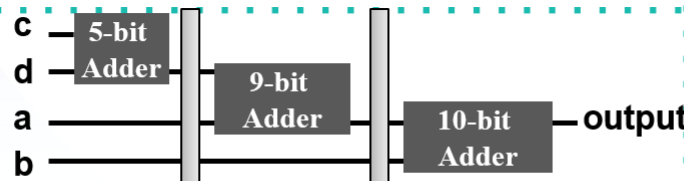

Area: 24 units+reg

Time: $10 \times 1002 = 10020$
units



Outline

- ✓ Section 1- Timing
- ✓ **Section 2- Designware**



Overview of DesignWare

✓ IP (Intellectual Property)

- Soft IP : RTL design, requires verification.
- Firm IP : Netlist resource, less used.
- Hard IP : GDSII format, high performance but technology dependent.

✓ DesignWare library

- Provides synthesizable and verification IPs.
- Supports the method to optimize the area or the speed and reduce the timing.

✓ DesignWare IP library categories

- Building Block IPs (formally called Foundation Library)
- CoreTools
- Implementation IPs
- Smart Model Library
- Memory Models
- AMBA OCB Family
- Verification IPs



DesignWare Building Block IPs (1/2)

✓ DesignWare building block IPs

- A collection of reusable IP blocks integrated into the SYNOPSIS synthesis environment.

✓ Characteristics

- Pre-verified for quality and better quality of results (QOR) in synthesis, decreasing design and technology risk.
- Allows high-level optimization of performance during synthesis.
- Increased design reusability, productivity
- Parameterized in size and also in functionality for some IP
- Provide synthesizable models, simulation models, datasheets, and examples.



DesignWare Building Block IPs (2/2)

✓ Library categories

- Basic Library : A set of components bundled with HDL Compiler that implements several common arithmetic and logic functions.
- Logic : Combinational and sequential components
- Math : Arithmetic and trigonometric components
- Memory : Registers, FIFOs, and FIFO controllers, sync. And async. RAMs and stack components.
- DSP Library : Digital filters for digital signal processing (DSP) applications, ex: FIR, IIR filter
- Application Specific: Data integrity, interface, and JTAG components.
- GTECH Library : Genetic technology library, a technology-Independent, gate-level library.



Usage of DesignWare Building Block IP

✓ Usage of DesignWare Building Block IP

- Operator inference
 - Supply default function only, can not use special function.
- Instantiate IP
 - Use SYNOPSIS design compiler shell script.
 - Supply different architecture for implementation.
 - Applying pre-compiling sub-blocks speeds up the synthesis for large design.



Operator Inference (1/3)

✓ Operator inference

- Use the HDL operator in description, and the operator must include in *synthetic operator* definition.
- HDL compiler will infer synthetic operator in HDL code.
- HDL compiler supply high-level synthesis.
- The " / " operator is required for the DesignWare license.
- The HDL operator defined in standard synthetic operator:

Synthetic Operators	HDL Operator
adder	+, +1
subtractor	-, -1
comparator	==, <, <=, >, >=
multiplier	*
selector	If, case




Operator Inference (2/3)

✓ High-level synthesis

– Arithmetic optimization

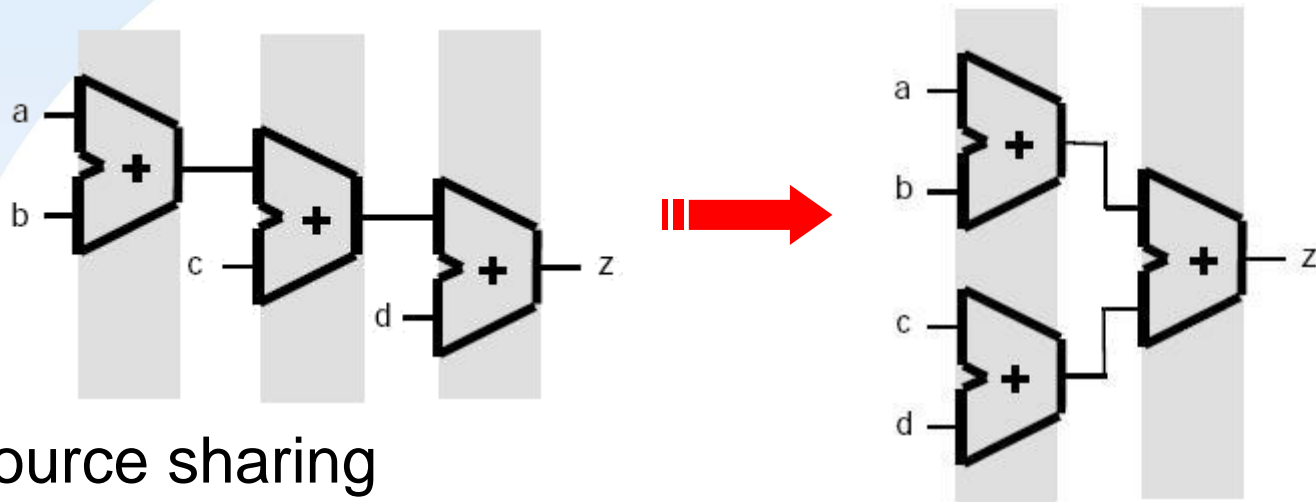- Arithmetic level optimization, ex: $a+b+c+d \rightarrow (a+b)+(c+d)$



– Resource sharing

- Allows similar operations that do not overlap in time to be carried out by the same physical hardware.

Operator inference (3/3)

✓ High-level synthesis flow


Your HDL Source Code

Operator Inference

Synthetic Operator

Automatic Implementation Selection
Based on Overall Design Constraints

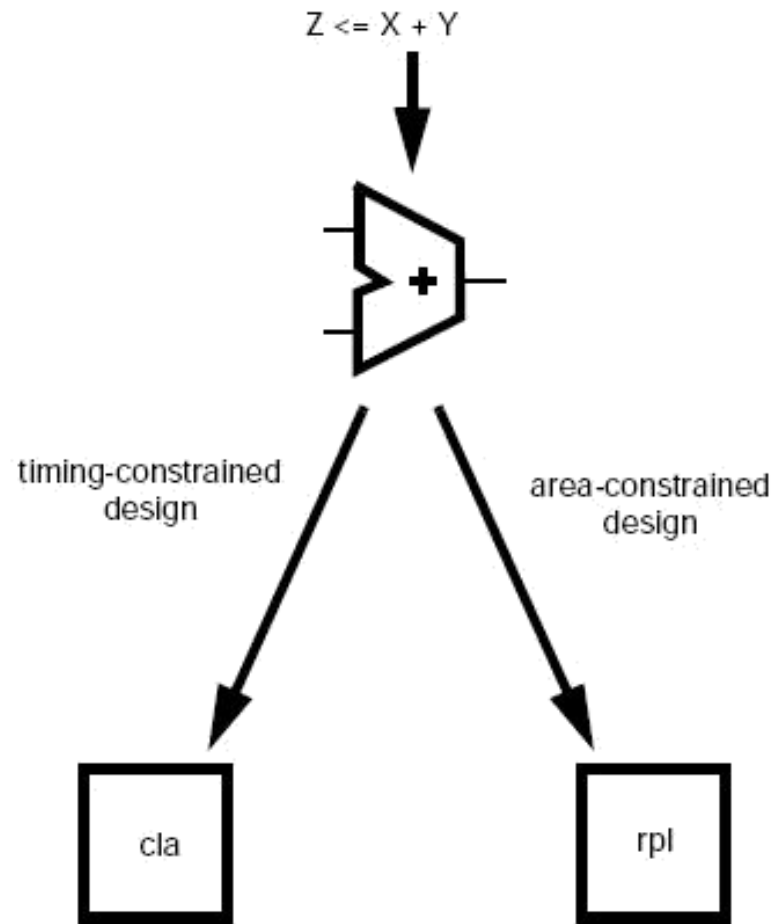Appropriate Implementation
Selected in Each Case



Instantiate IP (1/9)

✓ Instantiation IP

- To instantiate a synthetic module manually and explicitly.
- Need to include a reference to the synthetic module in HDL code.

✓ SYNOPSYS online document

- Command:

```
evince /usr/cad/synopsys/synthesis/cur/dw/doc/manuals/dwbb_userguide.pdf &
```



Instantiate IP (2/9)

- ✓ **SYNOPSYS online document**
 - Select section2.0

SYNOPSYS®

**DesignWare® Building Block IP
User Guide**

DesignWare Building Blocks — Product Code: 2925-0



Contents

Revision History	5
Preface	7
Chapter 1	
Introduction	9
1.1 Features and Benefits	10
1.2 License Requirements	11
1.3 Documentation	11
1.4 File Structure	12
1.5 DesignWare Library for DWBB	13
1.6 Synthesis Optimization Flow	14
1.7 minPower Overview	15
Chapter 2	
DWBB Components	17
Appendix A	
Standard Synthetic Operators	27
Appendix B	
minPower Components By Category	29

Go to page 14

Instantiate IP (3/9)

2

DWBB Components


Table 2-1 summarizes all DWBB components and provides a link to the detailed datasheet.

Datasheets include coding examples for instantiation, as well as for operator and function inference, where appropriate.

Table 2-1 List of DesignWare Building Block IP

Component	Inference?	Description
Application Specific: Control Logic		
DW_arb_2t	No	Two-Tier Arbiter with Dynamic/Fair-Among-Equal Scheme
DW_arb_dp	No	Arbiter with Dynamic Priority Scheme
DW_arb_fcfs	No	Arbiter with First-Come-First-Served Priority Scheme
DW_arb_rr	No	Arbiter with Round Robin Priority Scheme
DW_arb_sp	No	Arbiter with Static Priority Scheme
Datapath: Arithmetic Components		
DW01_absval	Function	Absolute Value
DW01_add	Operator	Adder
DW01_addsub	Operator	Adder-Subtractor
DW_addsub_dx	No	Duplex Adder/Subtractor with Saturation and Rounding
DW01_ash	Function	Arithmetic Shifter
DW_bin2gray	Function	Binary to Gray Converter

Instantiate IP (4/9)

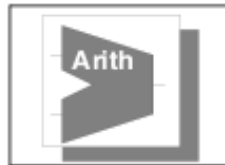

DW02_mult

Module name

Multiplier

Version, STAR and Download Information: [IP Directory](#)

Features and Benefits

- Parameterized word length
- Unsigned and signed (two's-complement) data operation

Description

DW02_mult is a multiplier that multiplies the operand *A* by *B* to produce the output, *PRODUCT*.

The control signal *TC* determines whether the input and output data is interpreted as unsigned (*TC*=0) or signed (*TC*=1) numbers.

 


Table 1-1 Pin Description

Pin Name	Width	Direction	Function
A	<i>A_width</i> bit(s)	Input	Multiplier
B	<i>B_width</i> bit(s)	Input	Multiplicand
TC	1 bit	Input	Two's complement control 0 = unsigned 1 = signed
PRODUCT	<i>A_width</i> + <i>B_width</i> bit(s)	Output	Product $A \times B$

input & output

Argument assignment:
DW02_mult #(N,N)
mult01(..., ..., ..., ...);

Table 1-2 Parameter Description

Parameter	Values	Description
<i>A_width</i>	≥ 1	Word length of A
<i>B_width</i>	≥ 1	Word length of B



Instantiate IP (5/9)

Table 1-3 Synthesis Implementations

Implementation Name	Function	License Feature Required
csa ^a	Carry-save array synthesis model	none
pparch ^b	Delay-optimized flexible Booth Wallace	DesignWare
apparch ^b	Area-optimized flexible Booth Wallace	DesignWare

User implementation type specification

Table 1-4 Simulation Models

Model	Function
DW02.DW02_MULT_CFG_SIM	Design unit name for VHDL simulation
dw/dw02/src/DW02_mult_sim.vhd	VHDL simulation model source code
dw/sim_ver/DW02_mult.v	Verilog simulation model source code

Simulation model path specification

Table 1-5 Functional Description

TC	A	B	PRODUCT
0	A (unsigned)	B (unsigned)	$A \times B$ (unsigned)
1	A (two's complement)	B (two's complement)	$A \times B$ (two's complement)

Functional parameter specification

Instantiate IP (6/9)

✓ Instantiate module

- Instantiate the synthetic module and specify parameters defined in document.

HDL Usage Through Component Instantiation - Verilog

```
module DW02_mult_inst( inst_A, inst_B, inst_TC, PRODUCT_inst );  
  
    parameter A_width = 8;  
    parameter B_width = 8;  
  
    input [A_width-1 : 0] inst_A;  
    input [B_width-1 : 0] inst_B;  
    input inst_TC;  
    output [A_width+B_width-1 : 0] PRODUCT_inst;  
  
    // Instance of DW02_mult  
    DW02_mult #(A_width, B_width)  
        U1 ( .A(inst_A), .B(inst_B), .TC(inst_TC), .PRODUCT(PRODUCT_inst) );  
  
endmodule
```

Table1-2

Table1-1 I/O port



Instantiate IP (7/9)

✓ RTL behavior simulation

- Specify the behavioral simulation models (Table1-4).
 - Absolute path
 - Relative path

✓ Absolute path

- ``include "/usr/synthesis/dw/sim_ver/<model_name>.v "`

```
`include /usr/synthesis/dw/sim_ver/DW02_mult.v“
```

✓ Relative path

- ``include "<model_name>.v "`

```
`include "DW02_mult.v“
```

- Command: `irun <file_name>.v –incdir <directory>`
 - Ex : `irun DW02_multi_inst.v –incdir /usr/synthesis/dw/sim_ver/`



Instantiate IP (7/9)

```
VCS_RTL_SIM = vcs ${TIMESCALE} \  
    -j${num_CPU_cores} \  
    -sverilog \  
    +v2k \  
    -full64 \  
    -Mupdate \  
    -R \  
    -debug_access+all \  
    -y ${DW_SIM} \  
    +libext+.v \  
    -f ${source_file} \  
    -o ${output_file} \  
    -l ${log_file} \  
    -P ${VERDI}/share/PLI/VCS/linux64/novas.tab \  
    ${VERDI}/share/PLI/VCS/linux64/pli.a \  
    +define+RTL \  
    +notimingchecks
```



Instantiate IP (8/9)

✓ Synthesis

- Apply `//synopsys translate_off`
`//synopsys translate_on`

```
//synopsys translate_off (DA synthesis off)
..... (the code won't be synthesis)
//synopsys translate_on (DA synthesis on)
```

✓ Set the implementation type of IP

- User specify the implementation type of IP manually.

```
.....
//synopsys dc_script_begin
//set_implementation wall U1 (instance name of IP)
implementation type from (Table1-3)
//synopsys dc_script_end
.....
```



Instantiate IP (9/9)

✓ Example

- RTL/Gate simulation description

```
module SignedMultiplier(a, b, product);  
  input [7 : 0] a;  
  input [7 : 0] b;  
  output [15: 0] product;  
  
  DW02_mult  #(8, 8)  U1 (.A(a), .B(b), .TC(1'b1), .PRODUCT(product));  
  (cell name)  (Table1-2)                      (Table1-1)  
  
  //synopsys dc_script_begin  
  //set_implementation csa U1  
  (Table1-3)  
  //synopsys dc_script_end  
  
endmodule
```



Reference

- ✓ https://blog.51cto.com/u_15076209/4702482?fbclid=IwAR3V4tEEPMQ_NJKI-2AFvaEksIUzPBvww5E7yqvpRDmujNUTkDat7bBCKQ0
- ✓ https://zhuanlan.zhihu.com/p/278523793?fbclid=IwAR2W0cuazZ8Ci5G_C1QCMDMiBqBC42YasmEW67hLJZuaRdU6VeCPjOuoYgE

