

# NCTU-EE IC LAB – Fall 2023

## Lab02 Practice

### Design: Complex Number Calculator

#### Data Preparation

---

1. Extract test data from TA's directory:  
`% tar xvf ~iclabTA01/Lab02.tar`
2. The extracted LAB director contains:
  - a. Exercise
  - b. Practice

#### Design Description

---

Complex numbers are widely used in engineering field, such as communications, circuit designs, or waveform analysis. A complex number contains a real part  $a$  and an imaginary part  $b$ , which can be denoted in  $a+bi$ . Now you are going to implement a complex number calculator, which can perform addition, subtraction and multiplication to two complex numbers  $a+bi$  and  $c+di$ . The arithmetic result  $e+fi$  will be: addition:  $(a+c) + (b+d)i$ , subtraction:  $(a-c) + (b-d)i$ , and multiplication:  $(ac-bd) + (ad+bc)i$ . Try to implement the calculator as small as possible.

#### Inputs

---

1. You will receive a sequence of 8-bit 2's complement *signed numbers* **IN[7:0]** with length 4, representing **a**, **b**, **c** and **d** in order sequentially. The input values' range is -128~127.
2. The sequence with length 4 is valid when **IN\_VALID** is high.
3. **MODE** is valid when the *first cycle* of **IN\_VALID** is high.  
MODE 0: **Addition**  
MODE 1: **Subtraction**  
MODE 2: **Multiplication**
4. There is *only 1 reset* before the first pattern, thus, your design must be able to reset automatically.
5. All inputs will be changed at clock *negative* edge.
6. The next input pattern will come in 1~3 cycles after **OUT\_VALID** falls.

## Outputs

1. You have to output a sequence of 17-bit **2's complement signed numbers** **OUT[16:0]** in consecutive 2 cycles, representing **e** and **f** respectively.
2. All outputs are synchronized at clock **positive** edge.
3. **OUT\_VALID** should be low after initial reset.
4. **OUT\_VALID** should not be raised when **IN\_VALID** is high.
5. **OUT\_VALID** is set to high when the output value is valid.
6. The test pattern will check whether your output sequence is correct or not at clock **negative** edge.

## Specifications

1. Top module name : **CNC** (File name : **CNC.v**)
2. Input pins: **clk, rst\_n, IN\_VALID, IN[7:0], MODE**
3. Output pins: **OUT\_VALID, OUT[16:0]**
4. It is **synchronous** reset and **active-low** architecture.
5. All numbers are represented in **2's complement signed number** format, so you have to do sign extension whenever necessary.
6. The latency of your design in each pattern should not be larger than **100** cycles. The latency is defined in Fig.1.
7. The clock period is set to **6ns**, and both input and output delay are set to **3ns**.
8. The output loading is set to 0.05.
9. The synthesis result of data type cannot include any **LATCH** (in syn.log).
10. After synthesis, you can check CNC.area, CNC.timing and CNC.resource.
11. The slack in the end of CNC.timing should be **non-negative** and the result should be **MET**.


Note: If you want to use signed multiplication, both two inputs of the multiplier should be declared with **signed**.

Ex:

```
reg signed [3:0] A;  
reg signed [3:0] B;  
reg [3:0] C;  
reg [7:0] OUT;
```

```
always @* OUT=A*B;           ← signed multiplication  
always @* OUT=A*C;           }  
always @* OUT={A[3], A[3:1]}*B; } ← unsigned multiplication  
always @* OUT=A*{1'b0, A[2:0]}; }
```

## Block Diagram

 

## Note

1. This practice is for practicing the finite state machine (FSM), thus some codes are given; try to complete the codes to achieve the correct result. However, you can implement the design with your own code.
2. Try to use as less hardware as possible.  
**Hint: Accumulator can be reused.**
3. Template folders and reference commands:  
01\_RTL/ (RTL simulation) **.01\_run**  
02\_SYN/ (Synthesis) **.01\_run\_dc**  
(Check the design which contains **Latch** or not in **syn.log**)  
(Check the design's timing in /Report/CNC.timing)  
03\_GATE\_SIM/ (GL simulation) **.01\_run**  
You can key in **.09\_clean\_up** to clear all log files and dump files in each folder
4. Sample waveform:

 


Fig.1